

14) With the initial condition $x(1) = 0.5$, the solution of the differential equation

$$t \frac{dx}{dt} + x = t$$

a) $x = t - \frac{1}{2}$

b) $x = t^2 - \frac{1}{2}$

c) $x = \frac{t^2}{2}$

d) $x = \frac{t}{2}$

15) The unilateral laplace transform of $f(t) = \frac{1}{s^2+s+1}$ is

a) $-\frac{s}{s^2+s+1^2}$

b) $-\frac{2s-1}{s^2+s+1^2}$

c) $\frac{s}{s^2+s+1^2}$

d) $\frac{2s-1}{s^2+s+1^2}$

16) The average power deliver to an impedance $(4 - j3)\omega$ by a current $5 \cos(100\pi t + 100)$


a) $44.2W$

b) $50W$

c) $62.5W$

d) $125W$

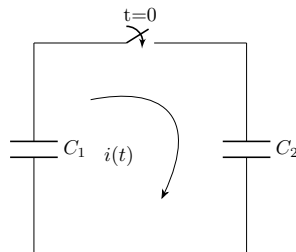17) In the following figure, C_1 and C_2 are ideal capacitors. C_1 has been charged to $12V$ before the ideal switch S is closed at $t = 0$. The current $i(t)$ for all t is



a) zero


b) a step function

c) an exponentially decaying function

d) an impulse function

c) Occurs when $CLK = 0$ and $A = B = 1$ d) Occurs when $CLK = 1$ and $A = B = 0$

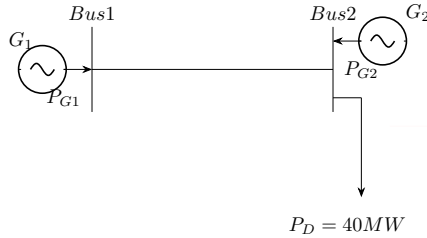- 21) The figure shows a two-generator system supplying a load of $P_D = 40MW$, connected at bus 2



The fuel costs of generators G_1, G_2 are:

$$C_1(P_{G1}) = 10,000Rs/MWh \text{ and } C_2(P_{G2}) = 12,500Rs/MWh$$

and the loss in the line $P_{loss(pu)} = 0.5P_{G1(pu)}^2$, where the loss coefficient is specified in pu on a 100MVA base. The most economic power generation schedule in MW is,

- a) $P_{G1} = 20, P_{G2} = 22$ b) $P_{G1} = 22, P_{G2} = 20$
c) $P_{G1} = 20, P_{G2} = 20$ d) $P_{G1} = 0, P_{G2} = 40$

- 22) The sequence of components in a fault current are as follows: $I_{positive} = j1.5pu, I_{negative} = -j0.5pu, I_{zero} = -j1pu$. The type of fault in the system is

- a) LG b) LL
c) LLG d) $LLLG$

- 23) A half-controlled single-phase bridge rectifier is supplying an $R-L$ load. It is operated at a firing angle α and the load current is continuous. The fraction of cycle that the freewheeling diode conducts is

- a) $\frac{1}{2}$ b) $1 - \frac{\alpha}{\pi}$
c) $\frac{\alpha}{2\pi}$ d) $\frac{\alpha}{\pi}$

- 24) The typical ratio of latching current to holding current in a 20A thyristor is

- a) 5.0 b) 2.0


c) 1.0

d) 0.5

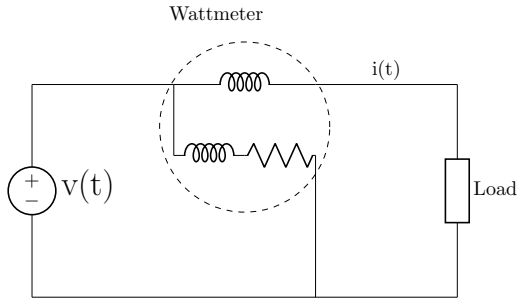25) For the circuit shown in the figure, the voltage and current expressions are

$$v(t) = E_1 \sin \omega t + E_3 \sin 3\omega t$$

$$i(t) = I_1 \sin \omega t - \phi_1 + I_3 \sin 3\omega t - \phi_3 + I_5 \sin 5\omega t$$



The average power measured by the wattmeter is

a) $\frac{1}{2} E_1 I_1 \cos \phi_1$

b) $\frac{1}{2} [E_1 I_1 \cos \phi_1 + E_1 I_3 \cos \phi_3 + E_1 I_5]$

c) $\frac{1}{2} [E_1 I_1 \cos \phi_1 + E_3 I_3 \cos \phi_3]$

d) $\frac{1}{2} [E_1 I_1 \cos \phi_1 + E_3 I_1 \cos \phi_1]$

26) Given that

$$\mathbf{A} = \begin{pmatrix} -5 & -3 \\ 2 & 0 \end{pmatrix}, \mathbf{I} = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}$$

the value of \mathbf{A}^3 is

a) $15\mathbf{A} + 12\mathbf{I}$

b) $19\mathbf{A} + 30\mathbf{I}$

c) $17\mathbf{A} + 15\mathbf{I}$

d) $17\mathbf{A} + 21\mathbf{I}$